

# Automating RF Circuit Synthesis

## EE4902 Presentation

Anirudh B S (EE21B019)

30th April 2024

# Motivation

- Role of a Designer
- Advantage of ML
- Why this project

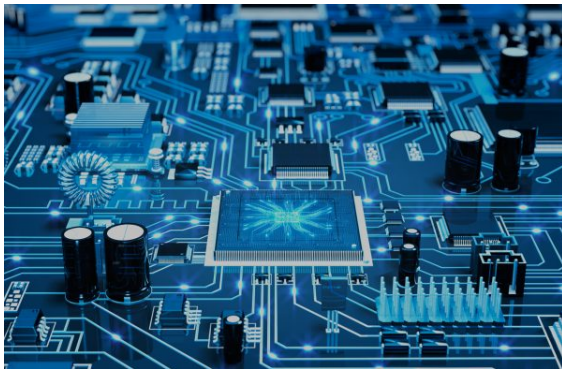


Figure: Ref : Automation Intellect

# Algorithm


- (1) Select the particular topology
- (2) Design the schematic in Cadence
- (3) Select the operating point. The local minima is highly influenced by the point chosen.
- (4) Extract out the netlist
- (5) Run the code specific to the netlist.
- (6) Run the sensitivity and PVT analysis on the netlists that have loss below a certain threshold.
- (7) Pick the netlist that satisfies the constraint on loss, sensitivity and PVT variations.

# Gradient Descent

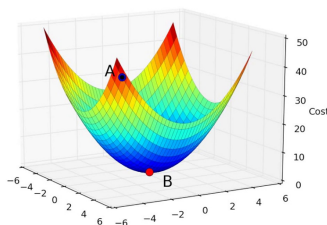- (1) Pick a starting point
- (2) Repeat until loss decreases in all dimensions
  - (a) Pick a direction
  - (b) Move incrementally in that direction

$$w_j = w_j - \eta \frac{d}{dw_j} \text{loss}(w)$$

where  $\eta$  is the popular **learning rate**



# Loss/ Objective Function


The objective function is a linear combination of the following

- (1) Gain Loss  $:= \text{ReLU}(\text{Gain specification} - \text{Gain simulated})$
- (2)  $IIP_3$  Loss  $:= \text{ReLU}(IIP_3 \text{ specification} - IIP_3 \text{ simulated})$
- (3)  $S_{11}$  Loss  $:= \text{ReLU}(S_{11} \text{ simulation} - S_{11} \text{ specification})$
- (4)  $I_{dd}$  Loss  $:= \text{ReLU}(I_{dd} \text{ simulation} - I_{dd} \text{ specification})$
- (5) NF Loss  $:= \text{ReLU}(\text{NF simulation} - \text{NF specification})$

$$\text{Loss} = \alpha_1 \text{ Gain Loss} + \alpha_2 IIP_3 \text{ Loss} + \alpha_3 \text{ NF Loss} + \alpha_4 S_{11} \text{ Loss} + \alpha_5 I_{dd} \text{ Loss}$$


# ReLU Activation

$$\text{ReLU}(x) = \max\{x, 0\}$$

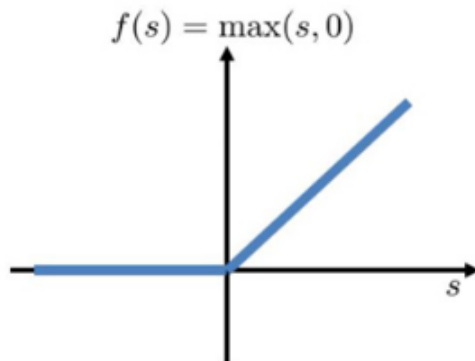

Rectified Linear Unit

# Noise Cancelling LNA - Schematic

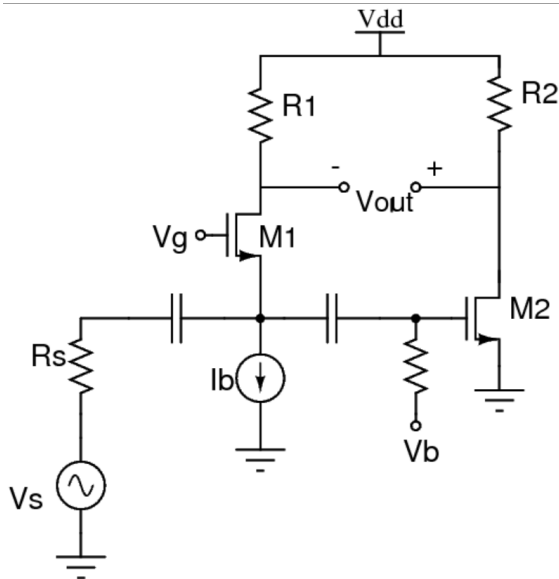

# Noise Cancelling LNA - Small Signal Analysis

## (1) $S_{11}$ Expression

$$Z_{in} = \frac{1}{g_{m1}} = R_s = 50\Omega; S_{11} = \frac{Z_{in} - R_s}{Z_{in} + R_s}$$

## (2) Noise Cancellation Condition

$$g_{m1}R_1 = g_{m2}R_2$$

## (3) Gain Expression

$$\frac{V_{out}}{V_{in}} = g_{m1}R_1 = g_{m2}R_2$$

## (4) Expression for Noise Figure

$$NF = 1 + \frac{R_s}{R_1} + \gamma \frac{R_2}{R_1} + \frac{R_s R_2}{R_1^2}$$

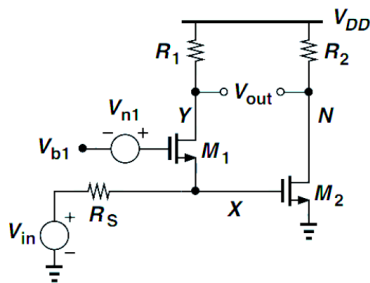


Figure: Noise Cancelling LNA



# Noise Cancelling LNA - Update Equations

If Gain Loss  $> 0$ :

$$R_1 \leftarrow R_1 + \alpha_1; R_2 \leftarrow R_2 + \alpha_1$$

If NF Loss  $> 0$ :

$$R_1 \leftarrow R_1 - \alpha_2; R_2 \leftarrow R_2 - \alpha_2$$

If  $I_{dd}$  Loss  $> 0$ :

$$m_s \leftarrow m_s + \alpha_1; m_g \leftarrow m_g + \alpha_1$$

If  $S_{11}$  Loss  $> 0$ :

$$m_g \leftarrow m_g + \alpha \frac{20}{m_g - 5}$$

If  $IIP_3$  Loss  $> 0$ :

$$m_s \leftarrow m_s - \alpha_2; m_g \leftarrow m_g - \alpha_2$$

where  $\alpha$ ,  $\alpha_1$  and  $\alpha_2$  are tunable hyperparameters called the **learning rate(s)**.

# Results

```
ee21b019@ams117~/EE4902/NoiseCancellingLNA/Demo> 50: python NCLNA.py
Parameters are {'ms': 20.0, 'mg': 80.0, 'R2': 500.0, 'R1': 200.0, 'Ib2': 0.0009,
'Ib1': 9.999999999999999e-06, 'VDD': 0.9, 'circ_temp': 27.0, 'frf': 100000000.0, 'prf': -40.0}
The DC operating point is :
Common Gate DCOP - gm : 0.008272424 S, gds : 0.0006486449 S, VDSAT : 0.1174172V

Common Source DCOP - gm : 0.02004698 S, gds : 0.0026513 S, VDSAT : 0.1138974V.
The current drawn from VDD is Idc = 0.001322653A
The power consumed is 0.0011903877 W
The AC gain at 1000000000.0 (in dB) is 15.825028840279941
The NF (in dB) at 1000000000.0 is 5.107236
The S11 (in dB) at 1000000000.0 is -17.5354 and the S21 (in dB) is 16.8219
IIP3 for a Input power of -40.0 is -7.084839398354831 dBm
The value of loss is 2.1085586530000002
```

Figure: Starting Netlist

```
sh-5.1$ tcsh
ee21b019@ams117~/EE4902/NoiseCancellingLNA/Demo> 50: python NCLNA.py
Parameters are {'ms': 107.0, 'mg': 167.0, 'R2': 500.0, 'R1': 200.0, 'Ib2': 0.0009, 'Ib1': 9.999999999999999e-06, 'VDD': 0.9,
'circ_temp': 27.0, 'frf': 1000000000.0, 'prf': -40.0}
The DC operating point is :
Common Gate DCOP - gm : 0.02589568 S, gds : 0.002214337 S, VDSAT : 0.1140186V
Common Source DCOP - gm : 0.02181379 S, gds : 0.003343131 S, VDSAT : 0.1127661V.
The current drawn from VDD is Idc = 0.002073518A
The power consumed is 0.0018661662 W
The AC gain at 1000000000.0 (in dB) is 18.937782761891576
The NF (in dB) at 1000000000.0 is 2.791482
The S11 (in dB) at 1000000000.0 is -13.8161 and the S21 (in dB) is 19.4971
IIP3 for a Input power of -40.0 is -3.848847164256057 dBm
The value of loss is 0.002073518
```


Figure: "Best" Netlist

# Noise Cancelling LNA - "Best" Netlist


```
61
62 ee21b019@ams117~/EE4902/NoiseCancellingLNA/Demo> 51: python NCLNA.py
63 For Netlist 0, the analysis is done below -
64 The loss at -40 degree C is 0.001938817
65 The loss at 0 degree C is 0.001970255
66 The loss at 27 degree C is 0.001990783
67 The loss at 100 degree C is 1.3920957329999992
68
69 The loss at TOP_TT process is 0.001990783
70 The loss at TOP_FF process is 0.002053277
71 The loss at TOP_FS process is 0.002039875
72 The loss at TOP_SF process is 0.07775088300000009
73 The loss at TOP_SS process is 0.139516461
74
75 The loss at 0.81V is 0.0068942460000000107
76 The loss at 0.9V is 0.001990783
77 The loss at 0.99V is 0.002081644
78
79 Sensitivity is 1.392699999999995e-05
80 Temperature Sensitivity is 2.0400000000017626e-07
81 ee21b019@ams117~/EE4902/NoiseCancellingLNA/Demo> 52:
```

Figure: Sensitivity and PVT Variations

# Loss - Noise Cancelling LNA

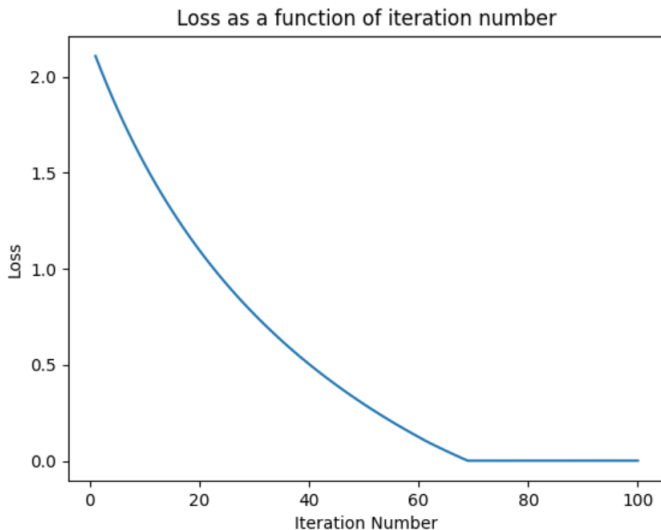

# Resistive Feedback LNA - Schematic

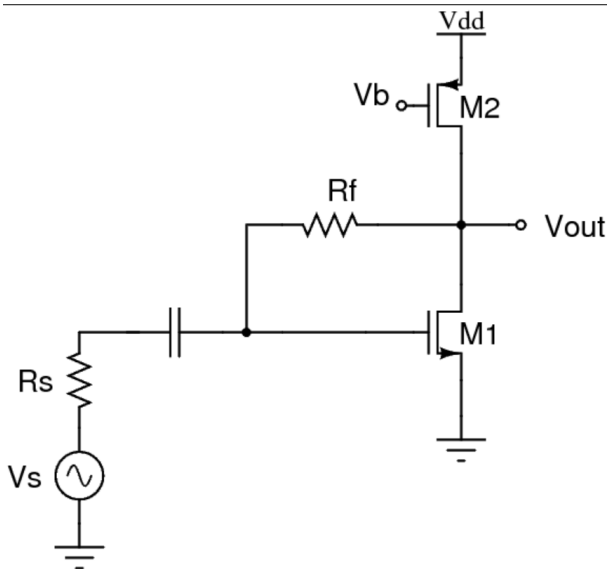

# Resistive Feedback LNA - Small Signal Analysis

## (1) $S_{11}$ Expression

$$Z_{in} = \frac{1}{g_{m1}} = R_s = 50\Omega$$

$$S_{11} = \frac{Z_{in} - R_s}{Z_{in} + R_s}$$

## (2) Gain Expression

$$\frac{V_{out}}{V_{in}} = \frac{1 - g_{m1}R_f}{1 + g_{m1}R_s} \approx -\frac{R_f}{R_s}$$

## (3) Expression for Noise Figure

$$NF \approx 1 + 4\frac{R_s}{R_f} + \gamma + \gamma g_{m2}R_s$$

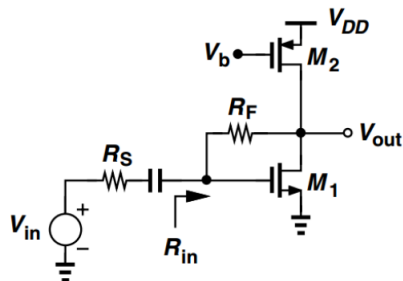


Figure: Resistive Feedback LNA

# Resistive Feedback LNA - Update Equations

If Gain Loss  $> 0$ :

$$R_f \leftarrow R_f + \alpha_1; m_1 \leftarrow m_1 + \alpha_1$$

If NF Loss  $> 0$ :

$$R_f \leftarrow R_f - \alpha_2$$

If  $I_{dd}$  Loss  $> 0$ :

$$m_1 \leftarrow m_1 + \alpha_1; m_2 \leftarrow m_2 + \alpha_1$$

If  $S_{11}$  Loss  $> 0$ :

$$m_1 \leftarrow m_1 + \alpha \frac{20}{m_g - 5}$$

If  $IIP_3$  Loss  $> 0$ :

$$m_s \leftarrow m_s - \alpha_2; m_g \leftarrow m_g - \alpha_2$$

where  $\alpha$ ,  $\alpha_1$  and  $\alpha_2$  are tunable hyperparameters called the **learning rate(s)**.

# Results

```
ee21b019@ams117~/EE4902/ResistiveFeedbackLNA/Demo> 51: python RFLNA.py
The DC operating point is
gm : 0.02190101 S, gds : 0.001843623 S and VDSAT = 0.125024 V.
The current drawn from VDD is Idc = 0.0014307 A
Power Dissipated is 0.0012876300000000001 W
The AC gain at 1580000000.0 (in dB) is 9.118456218389866
The NF (in dB) at 1580000000.0 is 4.802808
The S11 (in dB) at 1580000000.0 is -12.9387 and the S21 (in dB) is 10.8638
IIP3 for a Input power of -40.0 is -10.350428333446441 dBm
The value of loss is 1.6857824816101334
```

Figure: Starting Netlist

```
sh-5.1$ tcsh
ee21b019@ams117~/EE4902/ResistiveFeedbackLNA/Demo> 50: python RFLNA.py
The DC operating point is
gm : 0.01693128 S, gds : 0.001437814 S and VDSAT = 0.1187204 V.
The current drawn from VDD is Idc = 0.0009421553 A
Power Dissipated is 0.00084793977 W
The AC gain at 1580000000.0 (in dB) is 12.790373956174179
The NF (in dB) at 1580000000.0 is 3.693218
The S11 (in dB) at 1580000000.0 is -20.2214 and the S21 (in dB) is 13.3612
IIP3 for a Input power of -40.0 is -14.267927442457559 dBm
The value of loss is 0.0009421553
```

Figure: "Best" Netlist



# Resistive Feedback LNA - "Best" Netlist

```
Temperature Sensitivity is 5.282000000000333e-07
ee21b019@ams117~/EE4902/ResistiveFeedbackLNA/Demo> 51: python RFLNA.py
For Netlist 0, the analysis is done below -
The loss at -40 degree C is 0.19854634507161945
The loss at 0 degree C is 0.0008786305
The loss at 27 degree C is 0.0009421553
The loss at 100 degree C is 0.3666076430000001


The loss at TOP_TT process is 0.0009421553
The loss at TOP_FF process is 0.001318576
The loss at TOP_FS process is 0.0008671747
The loss at TOP_SF process is 0.001031206
The loss at TOP_SS process is 0.43451564890000005

The loss at 0.81V is 0.04293915619999983
The loss at 0.9V is 0.0009421553
The loss at 0.99V is 0.001157762

Sensitivity is 1.6298500000000047e-05
Temperature Sensitivity is 5.328000000000841e-07
ee21b019@ams117~/EE4902/ResistiveFeedbackLNA/Demo> 52: █
```

Figure: Sensitivity and PVT Variations

# Loss - Resistive Feedback LNA

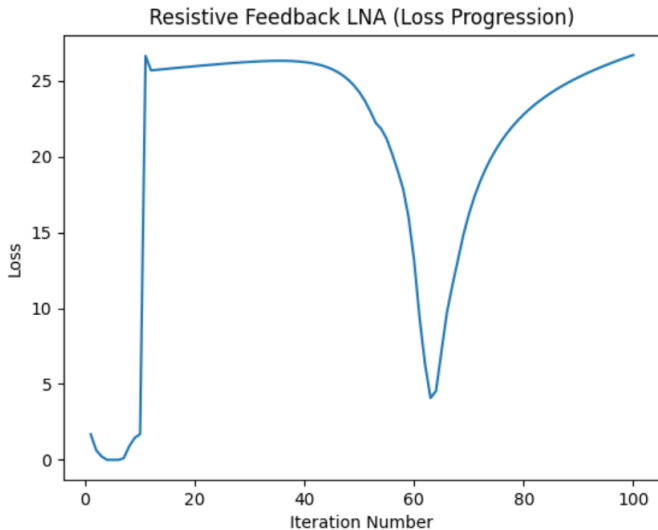

# Key Statistics

Property	Noise Cancelling	Resistive Feedback
Number of Iterations	100	100
Netlists passed Optimization	68	12
Netlists passed the PVT	32	3
Netlists passed Sensitivity	10	3
<b>Lowest Loss Obtained</b>	0.00199	0.0010
<b>Sensitivity</b>	$1.392 \times 10^{-5}$	$1.6298 \times 10^{-5}$

Table: Highlights

## Finally : The "best" Noise Cancelling LNA Netlist

Requirement	Specification	Starting Point	Final Result
Gain	15 dB	15.82 dB	18.85 dB
Noise Figure	5 dB	5.107 dB	2.938 dB
$S_{11}$	-10 dB	-17.5354 dB	-14.51 dB
$IIP_3$	-10 dBm	-7.08 dBm	-5.22 dBm
Power	Minimize	1.322 mW	1.79 mW
Loss		2.108	0.00199

Table: Noise Cancelling LNA - Results

The sensitivity was evaluated to be  $1.392 \times 10^{-5}$  while the temperature sensitivity evaluated to be  $2.04 \times 10^{-7}$ . The time taken to run this code was about 35 minutes.

## Finally : The "best" Resistive Feedback LNA Netlist

Requirement	Specification	Starting Point	Final Result
Gain	10 dB	9.11 dB	12.114 dB
Noise Figure	4 dB	4.80 dB	3.8133 dB
$S_{11}$	-10 dB	-12.94 dB	-18.8709 dB
$IIP_3$	-15 dBm	-10.35 dBm	-13.43 dBm
Power	Minimize	1.288 mW	0.95 mW
Loss		1.6857	0.0010

Table: Resistive Feedback LNA - Results

The sensitivity was evaluated to be  $1.62985 \times 10^{-5}$  while the temperature sensitivity evaluated to be  $5.328 \times 10^{-7}$ . The time taken to run this code was about 30 minutes.

# Conclusion

- The role of a designer is crucial and irreplaceable.
- Faster and easier to reach optimum
- Highly dependent on the initial netlist
- Cannot "generate" a netlist

**Thank You**